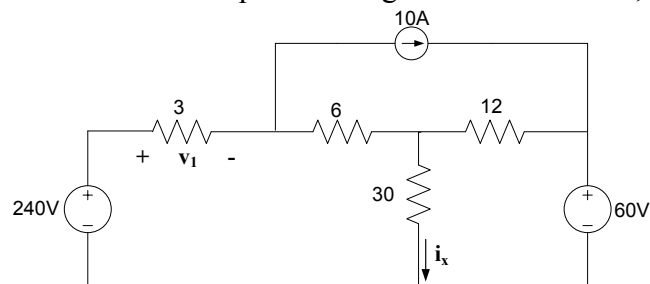


## TOPIC

Electricity and Magnetism – Section XI – Question 10

## QUESTION

The current in amperes through the  $30\ \Omega$  resistor,  $i_x$  most nearly is




- (A) 4.15
- (B) 10.00
- (C) 15.35
- (D) 19.50

## HINT

Kirchoff's voltage law (KVL) has already been presented in previous problems. KVL is a very useful technique to calculate unknown voltages. In addition, KVL can be extended to what is known as *Mesh Analysis* to calculate mesh currents in a circuit. There are two simple steps in performing mesh analysis;

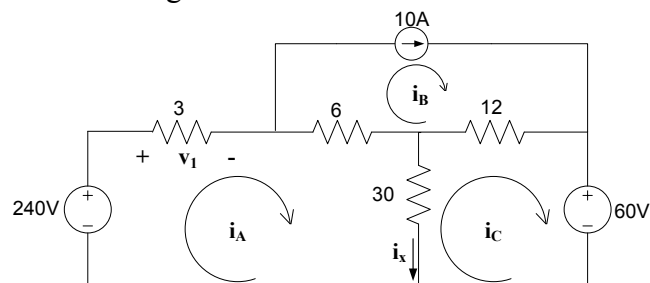1. Assign Clockwise Mesh Currents.

Think of meshes as independent territories or houses that are distinctively separated by fences. So, the following circuit has 3 meshes.



2. Add the voltages in every loop. Remember, from Ohm's law that

$$v = iR.$$

$$\text{KVL Mesh A: } -240 + 3i_A + 6(i_A - i_B) + 30(i_A - i_C) = 0$$

[when in mesh A then current  $i_A$  is dominant so it is  $i_A$  minus the rest].

KVL Mesh B:

$$i_B = 10$$

[On the top wire there is a current source so the current is known. Also, on that wire only mesh current  $i_B$  is traveling in the same direction. So, by inspection  $i_B = 10$ . *We perform mesh analysis to calculate the mesh currents. If we know the current then we do not perform a KVL equation in the mesh*].

KVL Mesh C:

$$30(i_C - i_A) + 12(i_C - i_B) + 60 = 0.$$

[When in mesh C then the current  $i_C$  is dominant so it is  $i_C$  minus the rest].

Substituting for  $i_B = 10$  and then simplifying and solving these two equations then

$$i_A = 19.5A$$

$$i_B = 10A$$

$$i_C = 15.35A.$$

## **CONTRIBUTOR**

Stelios Ioannou