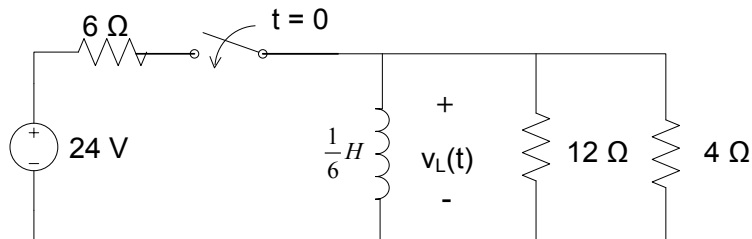


## TOPIC

Electricity and Magnetism – Section XI – Question 15

## QUESTION

The expression for the inductor voltage  $v_L(t)$  for  $t > 0$  is



- (A)  $-12e^{-18t}$
- (B)  $-2e^{-3t}$
- (C)  $4 - 4e^{-12t}$
- (D)  $8e^{-12t}$

## HINT

Also, note that the 12 Ω and the 4 Ω resistors are in parallel to the inductor. So, they have the same voltage drop across them. If the question was asking for the voltage drop across either of the two resistors then to keep things simple we would still solve for  $i_L(t)$  then differentiate to get  $v_L(t)$  and  $v_4(t) = v_{12}(t) = v_L(t)$ . Furthermore, the current through the 4 Ω resistor would be  $v_L(t)/4$  whereas the current through the 12 Ω resistor would be  $v_L(t)/12$ .

## CONTRIBUTOR

Stelios Ioannou