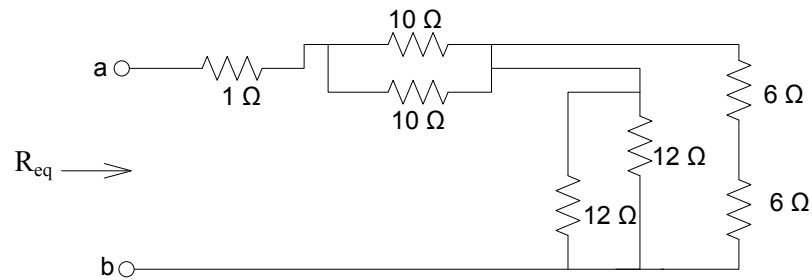


TOPIC

Electricity and Magnetism – Section XI – Question 8

QUESTION

The equivalent resistance in ohms of the circuit most nearly is



- (A) 0.93
- (B) 5.0
- (C) 10
- (D) 15

CONTRIBUTOR

Stelios Ioannou