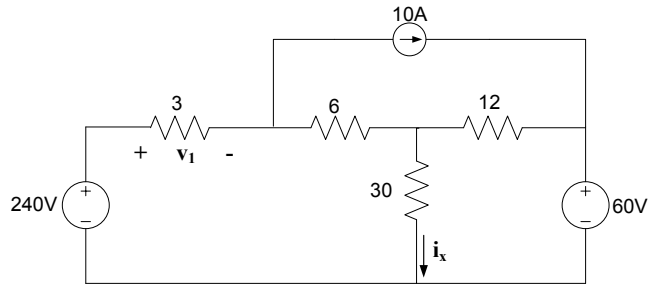


TOPIC

Electricity and Magnetism – Section XI – Question 10

QUESTIONThe current in amperes through the $30\ \Omega$ resistor, i_x most nearly is

- (A) 4.15
- (B) 10.00
- (C) 15.35
- (D) 19.50

CONTRIBUTOR

Stelios Ioannou