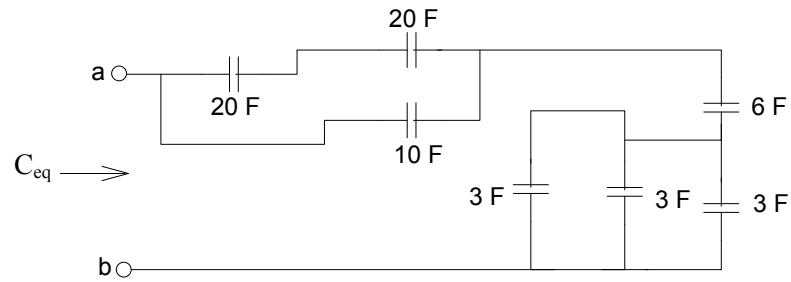


TOPIC

Electricity and Magnetism – Section XI – Question 11

QUESTION

The equivalent capacitance in Farads of the circuit below is most nearly



- (A) 3.051
- (B) 7.320
- (C) 15.00
- (D) 20.00

CONTRIBUTOR

Stelios Ioannou