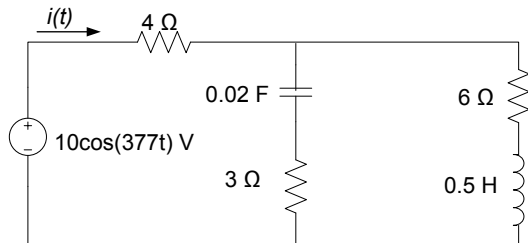


TOPIC

Electricity and Magnetism – Section XI – Question 18

QUESTION

The power factor (p.f.) for the following circuit most nearly is



- (A) -0.9737
- (B) 0.9737
- (C) -13.18
- (D) 13.18

CONTRIBUTOR

Stelios Ioannou