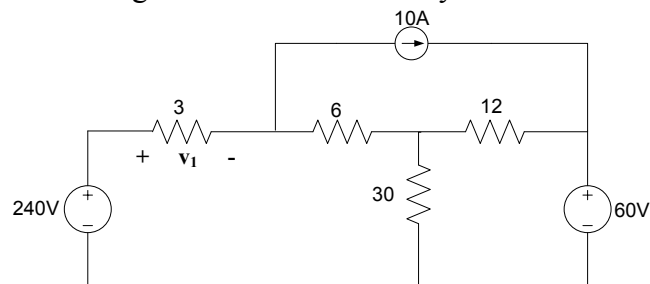


TOPIC

Electricity and Magnetism – Section XI – Question 9

QUESTION

The voltage v_1 in volts most nearly is




- (A) 58.50
- (B) 124.4
- (C) 181.5
- (D) 240.0

HINT

Kirchoff's current law (KCL) is a useful technique to calculate unknown currents. In addition KCL can be extended to what is known as *Nodal Analysis* to calculate nodal voltage in a circuit. There are three simple steps in performing nodal analysis;

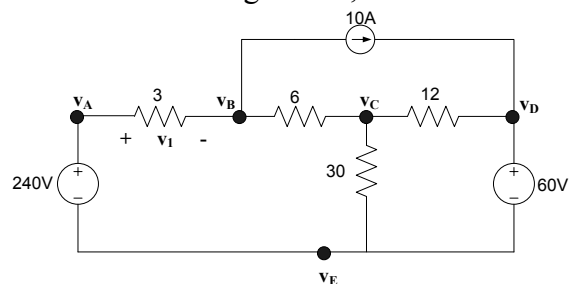1. Assign Nodal Voltages.

From the following circuit, 5 nodes show a system of 5 equations and 5 unknowns.



2. Pick a node and give it a known reference value. Keep things simple and make it a ground (zero volts).

SOLUTION

If we know a nodal voltage then we do not perform KCL on that node. Hence, by assigning $v_E=0V$ then instantly we have minimized our system to 4 equations and 4 unknowns. Usually, the bottom node is chosen or a node of a voltage source.

The advantage of choosing the ground at one side of a voltage source is that we can minimize our work even more. A voltage source or any voltage drop have polarity denoted by + and -. The positive it is the high potential whereas the negative is the low potential.

To illustrate this look at the 240V source. High potential is v_A and low potential is v_E . Hence, it can be said that

$$v_A - v_E = 240.$$

Similarly, for the 60V source


$$v_D - v_E = 60.$$

Also, the unknown voltage v_1

$$v_A - v_B = v_1.$$

Always remember that it is the high potential minus the low potential.

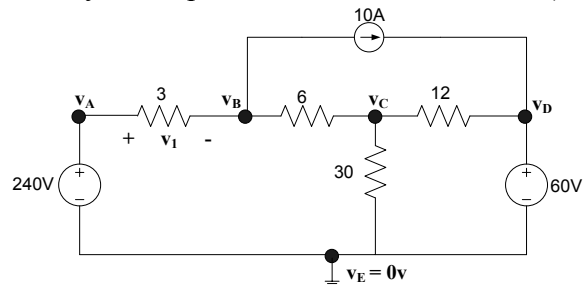Hence, by choosing $v_E = 0$, then $v_A = 240$ and $v_D = 60$. So, now the system is minimized even more to only two equations and two unknowns (v_B and v_C).



Sum the currents on every node. Remember, from Ohm's law that

$$i = v / R.$$

Assume that all currents are leaving the node unless if it is a current source. Currents entering a node are negative and currents leaving are positive.

$$\text{KCL at } v_B: \frac{v_B - v_A}{3} + \frac{v_B - v_C}{6} + 10 = 0$$

$$\text{KCL at } v_C: \frac{v_C - v_B}{6} + \frac{v_C - v_E}{30} + \frac{v_C - v_D}{12} = 0$$

Simplifying these two equations and substituting for $v_A = 240$, $v_D = 60$ and $v_E = 0$ then:

$$2v_B - 480 + v_B - v_C + 60 = 0$$

gives

$$3v_B - v_C = 420 \tag{1}$$

and

$$10v_C - 10v_B + 2v_C - 0 + 5v_C - 300 = 0$$

gives

$$-10v_B + 17v_C = 300 \tag{2}$$

Solving equations (1) and (2), we get

$$v_B = 181.5 \text{ V and}$$

$$v_C = 124.4 \text{ V}$$

Then

$$\begin{aligned} v_1 &= v_A - v_B \\ &= 240 - 181.5 \\ &= 58.5 \text{ V} \end{aligned}$$

ANSWER

(A)

CONTRIBUTOR

Stelios Ioannou