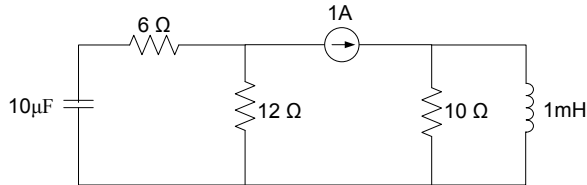


TOPIC

Electricity and Magnetism – Section XI – Question 13

QUESTION

The circuit below has been in the state for a long period. The energy stored in μJoules on the capacitor and inductor, respectively most nearly is



- (A) 0, 0
- (B) 5, 500
- (C) 720, 500
- (D) -720, 500

HINT


$$E_L = \frac{1}{2} L i_L^2 \text{ (The current through the inductor is required)}$$

$$E_C = \frac{1}{2} C V_C^2 \text{ (The voltage drop across the capacitor is required)}$$

For DC Signals: A capacitor is open circuit and an inductor is a short circuit.


SOLUTION

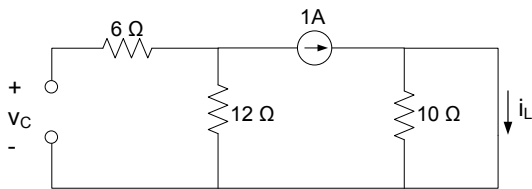The current source is DC. The capacitor is open circuit ($i_C=0\text{A}$) and the inductor is a short circuit ($v_L=0\text{v}$). Therefore, the circuit is as follows:



Analysis:

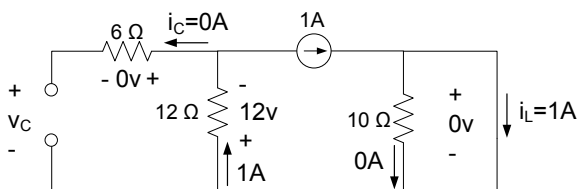The 10Ω resistor is in parallel to the inductor. So they have the same voltage drop. But the inductor is short circuit and $v_L=0$ which means that $v_{10}=0$. So the current through the 10Ω is $0/10=0\text{A}$.



So on the top right node, 1A is entering and 0A goes through the resistor which means that 1A goes through the inductor. Or KCL top node:

$$-1 + 0 + i_L = 0$$

$$i_L = 1\text{A.}$$

The current through the 6Ω resistor is the same with the capacitor current which is 0A . So, the voltage drop across the 6Ω resistor is 0v .

KVL left loop:

$$-v_C - 0 - 12 = 0$$

$$v_C = -12\text{V.}$$

$$E_L = \frac{1}{2}(1\text{m})(1)^2$$

$$= 0.5\text{mJ}$$

$$= 500\mu\text{J}$$

$$E_C = \frac{1}{2}(10\mu)(-12)^2$$

$$= 720\mu\text{J}$$

ANSWER

(C)

CONTRIBUTOR

Stelios Ioannou

